

## **Sallen-Key low pass filter LTspice simulation**

**Presented to DR.Fatma Mazen**

**Prepared by Mai Omar**

## ***Contents***

<b>1.Motivations.....</b>	
<b>2.Generalized Circuit Analysis.....</b>	
<b>3.Low-Pass Circuit.....</b>	
<b>4.Hand Analysis.....</b>	
<b>5. Simulation Results.....</b>	

## Motivations

The report gives a general overview Sallen-Key General Circuit analysis, followed by detailed discussions of low-pass , including design information, and Simulations.

---

### **1 Introduction**

Figure 1 shows a two-stage RC network that forms a second order low-pass filter. This filter is limited because its Q is always less than 1/2. With  $R_1=R_2$  and  $C_1=C_2$ ,  $Q=1/3$ . Q approaches the maximum value of 1/2 when the impedance of the second RC stage is much larger than the first. Most filters require Qs larger than 1/2.


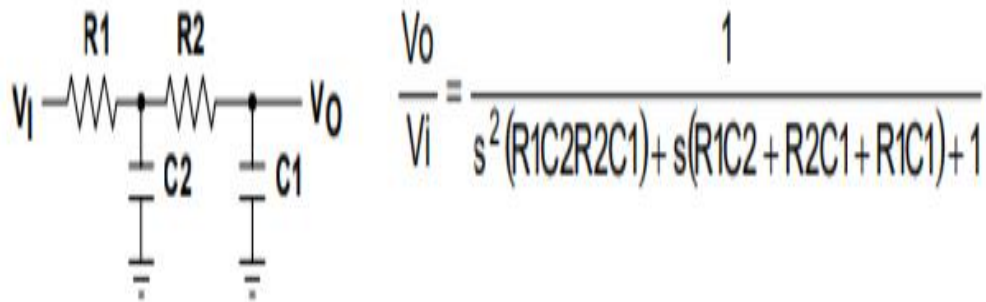


Figure 1. Basic Second Order Low-Pass Filter
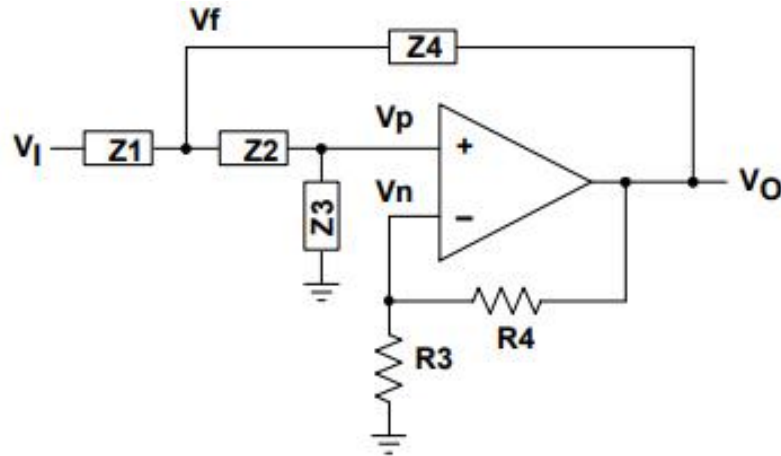
## Generalized Circuit Analysis

The circuit shown in Figure 2 is a generalized form of the Sallen-Key circuit, where generalized impedance terms,  $Z$ , are used for the passive filter components, and  $R3$  and  $R4$  set the pass-band gain



To find the circuit solution for this generalized circuit, find the mathematical relationships between  $V_i$ ,  $V_o$ ,  $V_p$ , and  $V_n$ , and construct a block diagram. KCL at  $V_f$ :  $V_f Z1$

**KCL at  $V_f$ :**

$$V_f \left( \frac{1}{Z1} + \frac{1}{Z2} + \frac{1}{Z4} \right) = V_i \left( \frac{1}{Z1} \right) + V_p \left( \frac{1}{Z2} \right) + V_o \left( \frac{1}{Z4} \right)$$

**KCL at  $V_p$ :**

$$V_p \left( \frac{1}{Z2} + \frac{1}{Z3} \right) = V_f \left( \frac{1}{Z2} \right) \Rightarrow V_f = V_p \left( 1 + \frac{Z2}{Z3} \right)$$


Substitute Equation (2) into Equation (1) and solve for  $V_p$ :

$$V_p = V_i \left( \frac{Z2Z3Z4}{Z2Z3Z4 + Z1Z2Z4 + Z1Z2Z3 + Z2Z2Z4 + Z2Z2Z1} \right) + V_o \left( \frac{Z1Z2Z3}{Z2Z3Z4 + Z1Z2Z4 + Z1Z2Z3 + Z2Z2Z4 + Z2Z2Z1} \right)$$

**KCL at  $V_n$ :**

$$V_n \left( \frac{1}{R3} + \frac{1}{R4} \right) = V_o \left( \frac{1}{R4} \right) \Rightarrow V_n = V_o \left( \frac{R3}{R3 + R4} \right)$$

### Low-Pass Sallen-Key Circuit

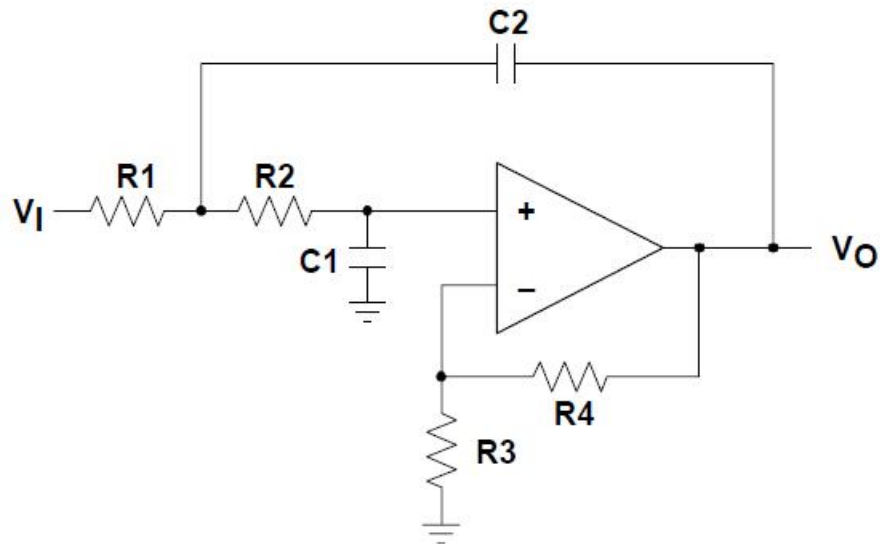

### Hand Analysis with Filter Components Equal

Letting  $R_1=R_2=R$ , and  $C_1=C_2=C$ , results in:


- 1-  $F_c = 1/2\pi RC$
- 2-  $W_o/Q = 3-k/RC$
- 3-  $W_o = 1/RC$

If we substitute with any Realizable Values for  $R, C$  we will get  $K$ .

$$K=1.58 \rightarrow 20\log(K)= 4\text{db}$$

## Simulation Results

### 1- Circuit

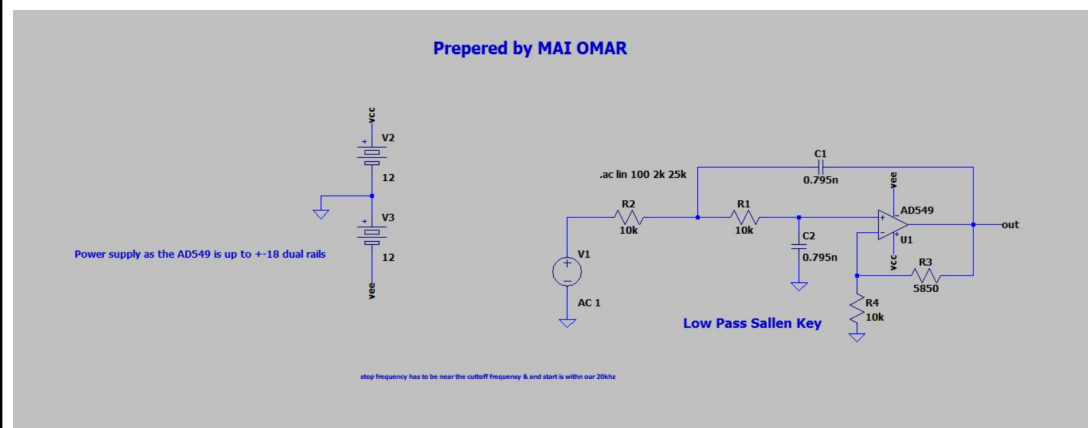

### 2- Putting $V_{in} = 1$ so gain = $V_{out}$ (Magnitude & Phase with cursor at 1db)

